


Exercises on boolean circuits

13/1/2012
E 11.1

 Exercise 1: Consider the boolean expression

$$E = (x_3 \wedge \neg((x_1 \vee x_2) \wedge (\neg x_1 \vee \neg x_2))) \vee (\neg x_3 \wedge (x_1 \vee x_2) \wedge (\neg x_1 \vee \neg x_2))$$

Construct a boolean circuit that computes the value of E , given inputs for x_1, x_2, x_3



what is the size of this circuit? 6 (¬ does not count)

what is the depth - " ? 4

How does the size compare to the length of E

Exercise: Reduction from Reachability to Circuit Value

E 11.2

Reachability: given a directed graph $G = (V, E)$
with $V = \{1, \dots, n\}$ and $E \subseteq V \times V$,
is there a path from node 1 to node n in G .

Circuit Value: given a boolean circuit C without input variables, is the output of C equal to T ?

We show a logspace reduction of Reachability to Circuit Value, i.e. we show how to construct in logspace from a directed graph G a circuit $R(G)$ such that:

1 is reachable from n in G iff
the value of $R(G)$ is T .

Notice that the key point is to compute $R(G)$ in logspace.


In $R(G)$ we use gates of two forms:

1) f_{ijk} , with $1 \leq i, j \leq n$ and $0 \leq k \leq n$

Intuitively, f_{ijk} is true iff $(i) \rightarrow \underbrace{O \rightarrow O \rightarrow \dots \rightarrow O}_{\text{all } \leq k} \rightarrow (j)$

i.e., there is a path from i to j not using any intermediate node bigger than k

 2) h_{ijk} , with $1 \leq i, j, k \leq n$ iff



i.e., there is a path from i to j not using any intermediate node bigger than k , but using k as intermediate node.

We describe now the gates and how they are connected.

- for $k=0$, all f_{ij0} gates are constant gates

$$f_{ij0} = T \quad \text{iff} \quad \left. \begin{array}{l} - i = j, \text{ or} \\ - i \rightarrow j \text{ in } G \end{array} \right\} \begin{array}{l} \text{This is how } G \\ \text{is reflected in} \\ R(G) \end{array}$$

(note that there are no h_{ij0} gates)

- for $k=1, 2, \dots, n$

- h_{ijk} is an AND gate with predecessors

$$f_{i,k,k-1} \quad \text{and} \quad f_{k,j,k-1}$$

- f_{ijk} is an OR gate with predecessors

$$f_{ij,k-1} \quad \text{and} \quad h_{ijk}$$

The output gate is $f_{n,n,n}$

Note that $R(G)$ can be computed from G in logarithmic space.

Note that the circuit $R(G)$ is legitimate, since it contains no cycles: we can rename the gates $1, 2, \dots, 2n^3 + n^2$,

- in non-decreasing order of the third index, and
- with h_{ijk} preceding f_{ijk}

We have to show that the value of the output gate of $R(G)$ is T iff there is a path from 1 to n in G .

We prove by induction on k that the values of the gates correspond to the informal meaning we gave them:

- for $k=0$: this holds
- if it is true up to $k-1$, the definitions of f_{ijk} and h_{ijk} guarantee that it is true also for k .

Exercise: A boolean function f is said to be monotone

if it has the following property: if one of the values changes from 0 to 1, then the value of f does not change from 1 to 0.

We show that f is monotone iff it can be expressed by a circuit with only AND and OR gates.

" \Leftarrow " Consider a circuit C with only AND and OR gates expressing f .

We show by induction on the depth of a node N :

- if the value of an input x changes from 0 to 1 then the value of N does not change from 1 to 0.

Base: $\text{depth}(N) = 0$, then N is either an input or a constant node.

- if it is a constant, its value does not change


- if it is an input different from x , - " -

- if it is input x , its value changes from 0 to 1 (and not from 1 to 0)


Induction: suppose that for all nodes at level k , the value does not change from 1 to 0.

Consider a node N at level $k+1$. We show that the value of N does not change from 1 to 0.

Case 1: N is an AND node

 

Case 2: N is an OR node

 

We need to consider various subcases, corresponding to the changes of y_1, y_2 from 0 to 1.

old		new		y _{AND}		y _{OR}	
y_1	y_2	y_1	y_2	old	new	old	new
0	0	1	1	0	1	0	1
0	0	1	0	0	0	0	1
0	0	0	1	0	0	0	1
0	1	1	1	0	0	1	1
1	0	1	1	0	0	1	1

We see that both for an AND node and for an OR node, the output value never changes from 1 to 0.

" \Rightarrow " We show by induction on n that every monotone boolean function $f(x_1, \dots, x_n)$ of n variables can be represented by a circuit with AND and OR gates only.

Base case: 0 arguments: f is constant, and hence monotone


Inductive case: assume the claim holds for n .

We show it holds for a function $f(x_1, \dots, x_{n+1})$.

We exploit the fact that

$$f(x_1, \dots, x_n, x_{n+1}) = (x_{n+1} \wedge f(x_1, \dots, x_n, 1)) \vee (\bar{x}_{n+1} \wedge f(x_1, \dots, x_n, 0))$$

 Hence, we can construct a circuit C_f computing $f(x_1, \dots, x_n, x_{n+1})$ as follows:




Observe that, since $f(x_1, \dots, x_{n+1})$ is monotone, we have that also $f(x_1, \dots, x_n, 0)$ and $f(x_1, \dots, x_n, 1)$ are monotone.

Hence, since $f(x_1, \dots, x_n, 0)$ and $f(x_1, \dots, x_n, 1)$ are n -variable monotone functions, by inductive hypothesis they can be represented by circuits with AND and OR gates only.

Hence, it suffices to show that we can get rid of the only remaining NOT gates.

 Consider the following circuit C_f' in which we have eliminated the NOT gates.



Let us consider the possible values of f in C_f and C'_f .
It depends on the values of x_n, v_0, v_1

	x_n	v_0	v_1	C_f	C'_f
1)	0	0	0	0	0
2)	0	0	1	0	0
3)	0	1	0	1	1
4)	0	1	1	1	1
5)	1	0	0	0	0
6)	1	0	1	1	1
7)	1	1	0	0	1
8)	1	1	1	1	1

Note that $C_f = C'_f$,
except for case (7).

However, since $f(x_1, \dots, x_{n+1})$ is monotone, cases (3) and (7) cannot occur, since they would mean that $f(x_1, \dots, x_n, x_{n+1})$ changes from $v_0 = 1$ for $x_{n+1} = 0$ to $v_1 = 0$ for $x_{n+1} = 1$.

Hence, C'_f is the correct circuit consisting of AND and OR gates only and computing $f(x_1, \dots, x_{n+1})$.